

- The implementation of half adder using **exclusive-OR** and an **AND** gates is used to show that two half adders can be used to construct a full adder.
- The inputs to the **XOR** gate are also the inputs to the **AND** gate.

2. Full Adder


Full Adder is a combinational circuit that performs the addition of three bits (two significant bits and previous carry).

- It consists of **three inputs and two outputs**, two inputs are the bits to be added, the third input represents the carry from the previous position.
- The full adder is usually a component in a cascade of adders, which add 8, 16, etc, binary numbers.

Inputs			Outputs	
<i>X</i>	<i>Y</i>	<i>C_{in}</i>	<i>S</i>	<i>C_{out}</i>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth table for the full adder

 - The **S** output is equal to **1** when only one input is equal to **1** or when all three inputs are equal to **1**.
- The **C_{out}** output has a carry **1** if two or three inputs are equal to **1**.
- The Karnaugh maps and the simplified expression are shown in the following figures:



$$\left. \begin{cases} S = \overline{X}\overline{Y}C_{in} + \overline{X}Y\overline{C}_{in} + X\overline{Y}\overline{C}_{in} + XYC_{in} \\ C_{out} = XY + XC_{in} + YC_{in} \end{cases} \right\} \text{1 (Sum of products)}$$