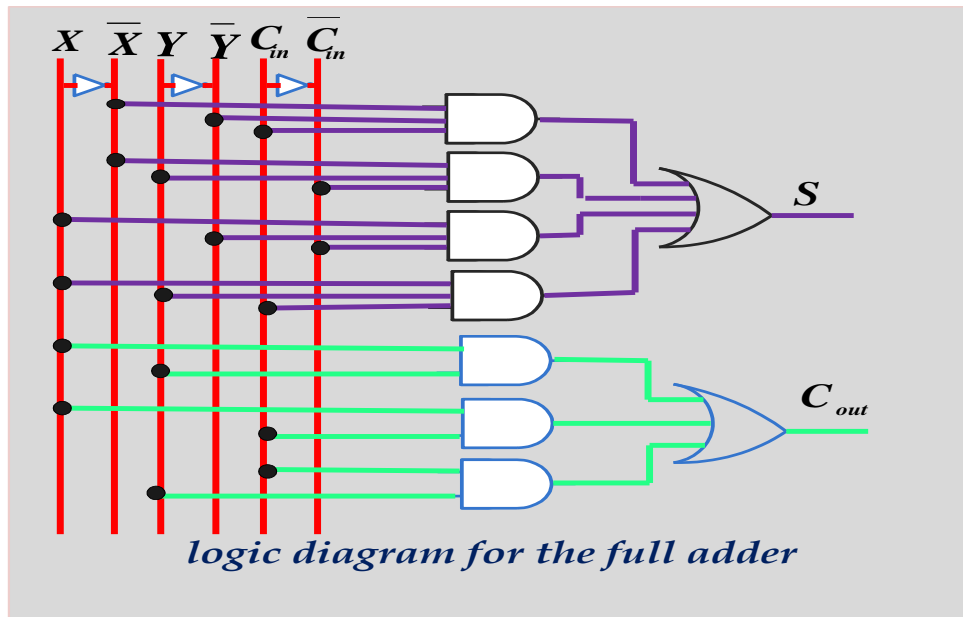


- The *logic diagrams* for the full adder implemented in *sum-of-products* form are the following:



- It can also be implemented using *two half adders* and *one OR gate* (using **XOR** gates).

$$\left\{ \begin{array}{l} S = C_{in} \oplus (X \oplus Y) \\ C_{out} = C_{in} \cdot (X \oplus Y) + XY \end{array} \right\}$$

Proof:

The sum:

$$\begin{aligned} S &= \bar{X}\bar{Y}C_{in} + \bar{X}Y\bar{C}_{in} + X\bar{Y}\bar{C}_{in} + XYC_{in} \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\bar{X}\bar{Y} + XY) \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\overline{\bar{X}Y + X\bar{Y}}) \\ S &= C_{in} \oplus (X \oplus Y) \end{aligned}$$

The carry output:

$$\begin{aligned} C_{out} &= \bar{X}Y C_{in} + X\bar{Y} C_{in} + XY C_{in} + XY \bar{C}_{in} \\ &= C_{in}(\bar{X}Y + X\bar{Y}) + XY(C_{in} + \bar{C}_{in}) \\ C_{out} &= C_{in} \cdot (X \oplus Y) + XY \end{aligned}$$